

1)

A half-bridge consisting of two nmos transistors is driving a capacitive load of 5 nF with a frequency of 100 kHz. The on-resistance of nmos transistors is 100 Ohm. The supply voltage is 10 V.

- a) Calculate the rise and fall time of the V_{DS} voltages.
- b) Calculate the VDS voltages of the nmos transistors.
- c) Calculate the switching loss of nmos transistors.